

Practical work n° 3 - Programmable timer

1 Goals

Implementation of an algorithm: decomposition into *data path* and *control unit* and generation of the corresponding VHDL model.

2 Specification

The programmable timer has

- one 4-bit input *delay*,
- four 1-bit inputs *clk*, *reset*, *start* and *reference*,
- one 1-bit output *done*

(figure 1).

 


Figure 1 Inputs and output

On every positive (0 to 1) transition of *start*, the circuit reads the value of *delay* and puts *done* at 0. After a time interval roughly equal to the period T of the *reference* signal, multiplied by the previously read value of *delay*, *done* goes from 0 to 1 (figure 2)

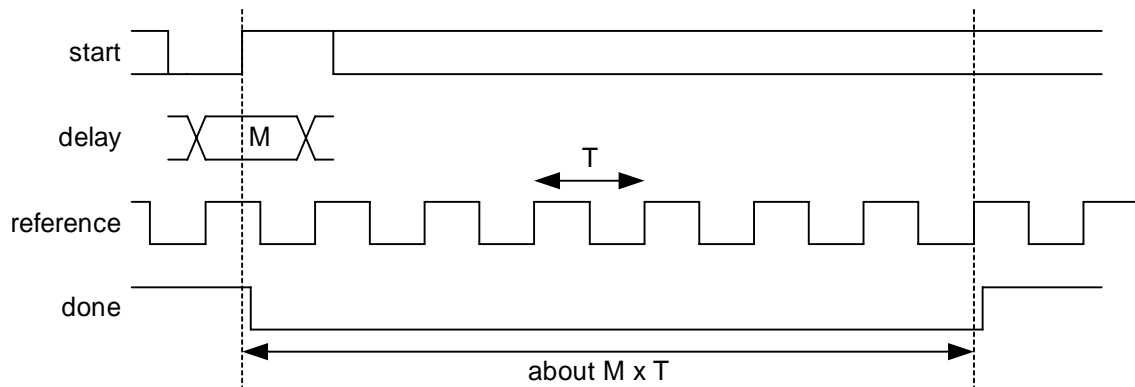


Figure 2 Timer working

The next algorithm describes the timer behavior:

```

while (1 == 1)
{
    while (start == 1); /* wait for start = 0
    while (start == 0); /* wait for a positive edge on start
    x = delay; done = 0; /* start up
    while (x > 0)
    {
        while (reference == 1); /* wait for reference = 0
        while (reference == 0); /* wait for a positive edge on
        /*reference
        x = x-1;
    }
    done = 1; /* end
}

```

The circuit is made up of a data path (figure 3) and a control unit (figure 4 and table 1).

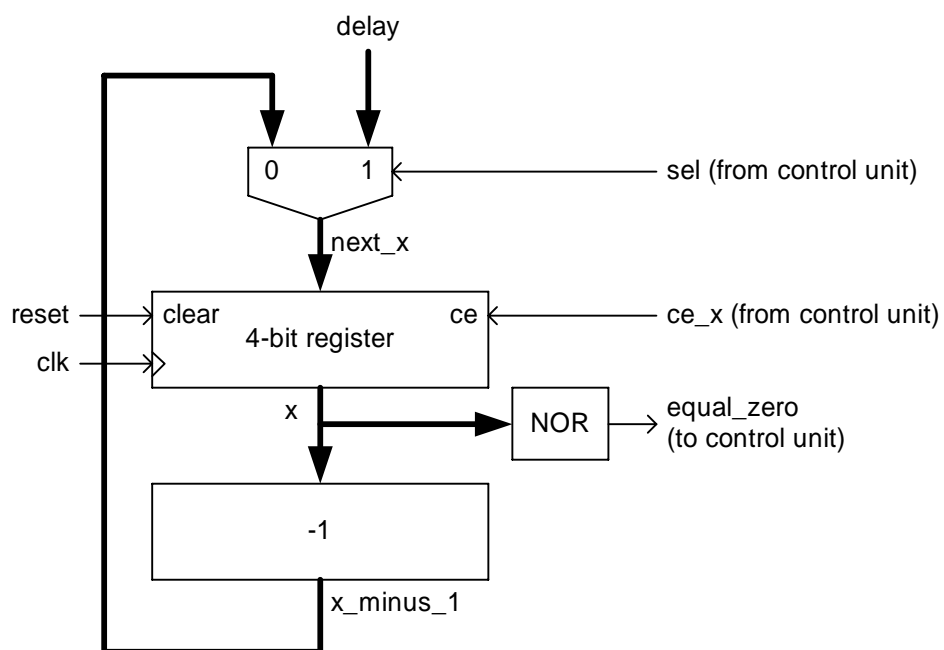


Figure 3 Data path

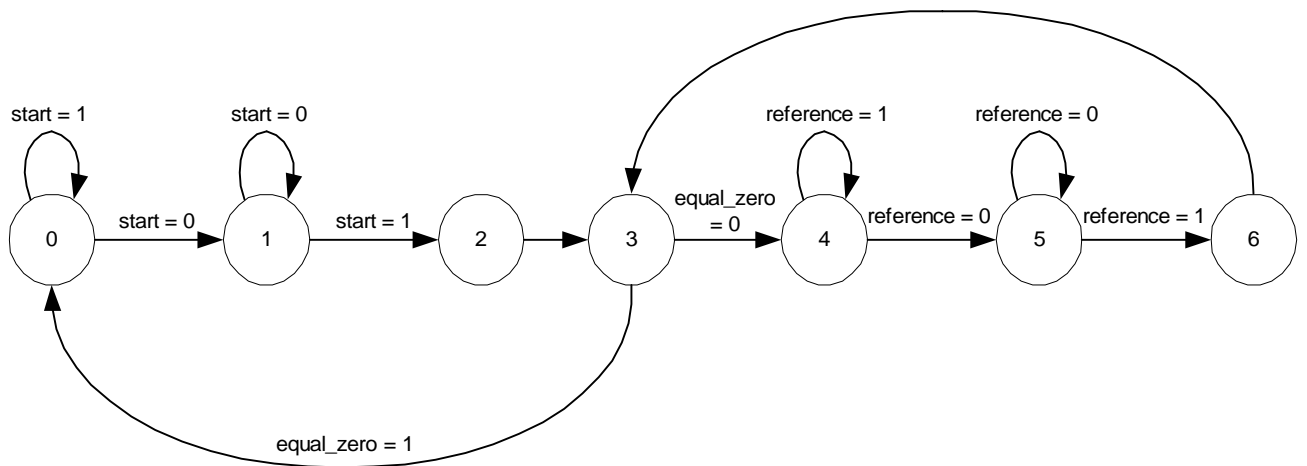


Figure 4 Control unit

| <i>state</i> | <i>operation</i> | <i>done</i> |
|--------------|------------------|-------------|
| 0 | nop | 1 |
| 1 | nop | 1 |
| 2 | x <= delay | 0 |
| 3 | nop | 0 |
| 4 | nop | 0 |
| 5 | nop | 0 |
| 6 | x <= x-1 | 0 |

Table 1 Operations and value of *done* in function of the control unit internal state

3 Previous work

3.1 Generate a VHDL model of the data path.

3.2 Generate a command file (.do) for simulating the data path.

3.3 Generate a VHDL model of the control unit.

3.4 Generate a command file for simulating the control unit.

3.5 Generate a VHDL model of the timer. For that purpose, use the data path and the control unit as components (figure 5).

3.6 Generate a command or test bench file for simulating the timer.

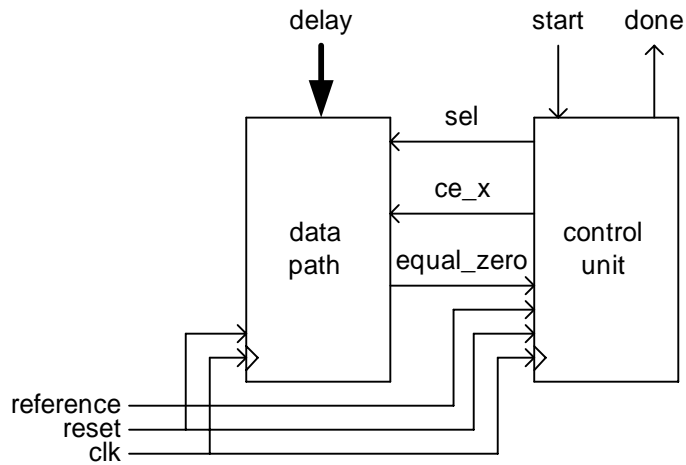


Figure 5 Timer

4 Practical work

- 4.1 Simulation of the data path, the control unit and the timer.
- 4.2 (optional) redesign the state machine using STATECad. Simulate.

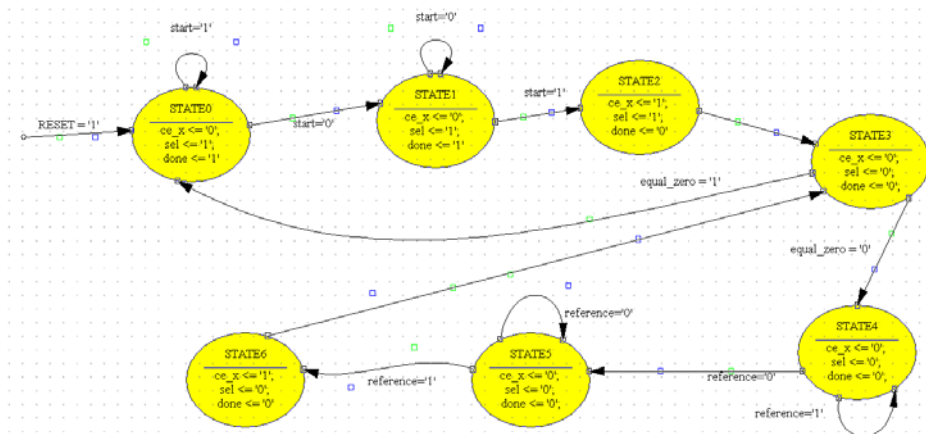


Figure 6 FSM designed with STATECad